

Homework 3

● Graded

Student

Ashley Leora Cain

Total Points

67 / 75 pts

Question 1

Datapath Tracing

28 / 28 pts

1.1 SW microcode

8 / 8 pts

✓ + 3 pts Asserts DrREG, LdA, LdB, RegSel=01, BrSel=1

✓ + 2 pts Asserts DrALU, LdMAR, func=00

✓ + 2 pts Asserts DrREG, WrMEM, RegSel=00

✓ + 1 pt Completed in three clock cycles

+ 4 pts Incorrect: Working SW except does not utilize BrSel

+ 0 pts Incorrect/blank/no answer

1.2 BEQ microcode

20 / 20 pts

✓ + 4 pts Asserted DrREG, LdA, RegSel = 00

✓ + 4 pts Asserted DrREG, LdB, RegSel = 01, BrSel = 0

✓ + 4 pts Asserted DrALU, LdCR, func = 01

✓ + 0 pts Asserted ChkCmp = 1 (Correct, but we are not requiring this triggered)

✓ + 4 pts Asserted DrPC, LdA, LdB, BrSel = 1

✓ + 4 pts Asserted DrALU, LdPC, func = 00

+ 0 pts Works and utilizes BrSel, but still uses more than 5 microstates (ignoring any ChkCmp only microstates)

+ 10 pts Works, but does not utilize BrSel at all

- 2 pts Second to last microstate broken up into 2 microstates and is thus inefficient

+ 0 pts Incorrect/Empty

Question 2

Datapath Design

16 / 16 pts

2.1 LC 2200 Bus Design

4 / 4 pts

✓ + 4 pts Correct

+ 0 pts Incorrect

2.2 Single-Bus vs Dual-Bus Design



Resolved

12 / 12 pts

+ 12 pts Correct

✓ + 6 pts Mentions a benefit of single-bus design (easier/simpler to implement, more flexibility to extend datapath because all components are connected to one another/can load multiple components at the same time, etc.)

✓ + 6 pts Mentions a drawback of single-bus design (more clock cycles because only one component can be writing at any given moment, etc.)

+ 0 pts Incorrect

+ 0 pts Incorrect/blank/no answer

💬 One instruction can be executed in multiple clock cycles

🔄 Regrade Request

Submitted on: Oct 06

2.2: I think that my answer should be counted correct since I mention that there can only be one piece of data on the bus at a time, which is stated in the grading rubric as a correct drawback
3.2: There should only be -4 points since I did have a correct instruction listed in BEQ4 and the grading rubric mentions only -4 points if "1 instruction correct"

Points returned.

Reviewed on: Oct 14

Question 3

Microcontroller Design

14 / 22 pts

3.1 Fetch microstates

4 / 4 pts

✓ - 0 pts Correct

fetch 3: 0000000011

lw1 : 0011000000

- 0 pts Do not take off points for the last five bits (intended answer: 00000 for fetch1; question wasn't clear)

- 0 pts Correct

- 1 pt Answer is reversed

- 1 pt Incorrect address size

- 1.5 pts Incorrect fifth bit (Z = 0)

- 2 pts Incorrect OpCode

- 2 pts Incorrect state bits

- 4 pts Incorrect

- 2 pts Incorrect fetch

3.2 BEQ microstates

Resolved 2 / 6 pts

- 0 pts Correct, Gave Microstates that output the T Bit (Beq3,4,5) (Correct answer)

- 0 pts Correct

- 6 pts Incorrect

- 0 pts Gave Microstates that require the T bit to be triggered (Beq4, 5, 6) (Accepted Answer)

- 2 pts Net 2 instructions correct (# Correct instructions - Incorrect)

✓ - 4 pts Net 1 instruction correct

- 6 pts Uncorrect

🔄 Regrade Request

Submitted on: Oct 06

2.2: I think that my answer should be counted correct since I mention that there can only be one piece of data on the bus at a time, which is stated in the grading rubric as a correct drawback

3.2: There should only be -4 points since I did have a correct instruction listed in BEQ4 and the grading rubric mentions only -4 points if "1 instruction correct"

Regraded

Reviewed on: Oct 15

3.3 — **M bit**

8 / 8 pts

✓ + 4 pts Describes that the M bit enables multiway branching for the end of fetch

✓ + 4 pts Describes that the M bit allows the microcontroller to read the OpCode

+ 2 pts Confuses the selection functionality with that of the T bit, where we append the Z-bit instead of the opcode.

+ 0 pts Blank/no answer

+ 0 pts Incorrect

3.4 — **Minimum bitsize of Next State Register**

0 / 4 pts

+ 4 pts Correct
(Largest instruction is BEQ, 6 microstates in total. Requires 3 bits to represent all the microstates)

+ 4 pts Correct

✓ + 0 pts Incorrect

Question 4

(no title)

6 / 6 pts

4.1 — (no title)

1 / 1 pt

✓ + 1 pt Correct

+ 0.5 pts Only Async

+ 0.5 pts Only Interrupt

+ 0 pts Incorrect

4.2 — (no title)

1 / 1 pt

✓ + 1 pt Correct

+ 0.5 pts Only Sync

+ 0.5 pts Only Exception

+ 0 pts Incorrect

4.3 — (no title)

1 / 1 pt

✓ + 1 pt Correct

+ 0.5 pts Only Sync

+ 0.5 pts Only Trap

+ 0 pts Incorrect

4.4 — (no title)

1 / 1 pt

✓ + 1 pt Correct

+ 0 pts Only Async

+ 0 pts Only Interrupt

+ 0 pts Incorrect

4.5 — (no title)

1 / 1 pt

✓ + 1 pt Correct

+ 0 pts Only Sync

+ 0 pts Only Exception

+ 0 pts Incorrect

4.6 (no title) 1 / 1 pt

✓ + 1 pt Correct

+ 0.5 pts Only Sync

+ 0.5 pts Only Trap

+ 0 pts Incorrect

Question 5

System vs. User Stack 3 / 3 pts

5.1 User Program 1 / 1 pt

✓ + 1 pt Correct

+ 0 pts Only User (Mode)

+ 0 pts Only User (Stack)

+ 0 pts Incorrect

5.2 Handler 1 1 / 1 pt

✓ + 1 pt Correct

+ 0 pts Only Kernel

+ 0 pts Only System

+ 0 pts Incorrect

5.3 After RTI(2) 1 / 1 pt

✓ + 1 pt Correct

+ 0 pts Only User (Mode)


+ 0 pts Only User (Stack)

+ 0 pts Incorrect

Q1 Datapath Tracing

28 Points

LC-5000 Datapath

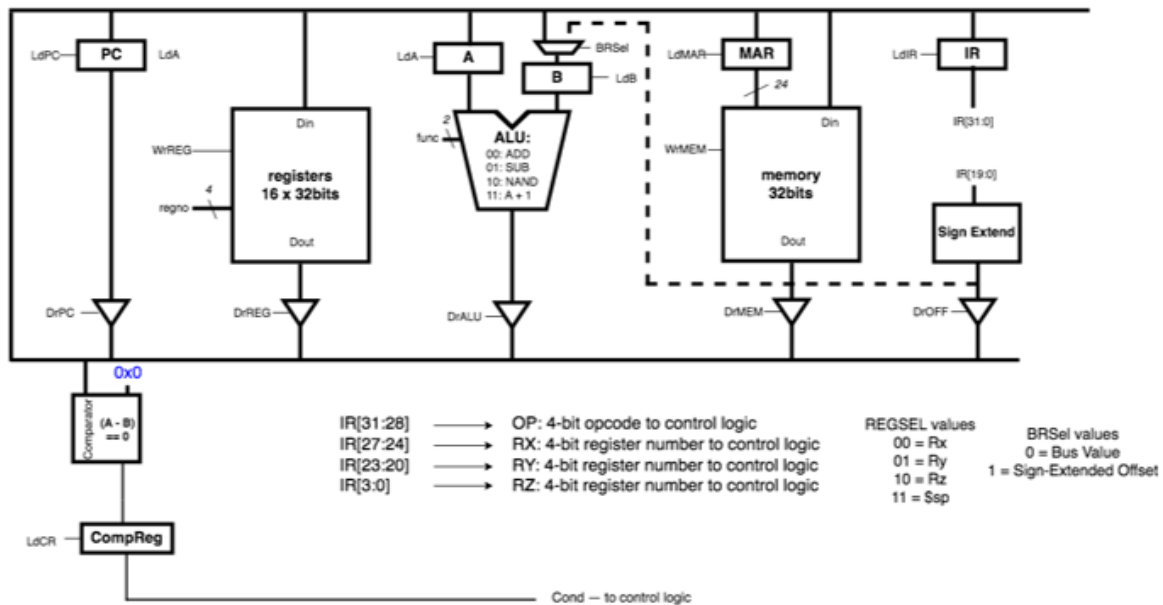

The above is the datapath of the LC-5000, a modified version of LC-2200. Notice the extra MUX north of the "B" register and a wire connecting the Sign Extend output to the new B mux. Also, note that the new mux uses control signals BRSel.

Q1.1 SW microcode

8 Points

Write out the microstates for an efficient **SW** instruction that makes use of the modifications on the LC-5000 datapath. This **SW** instruction accomplishes the same goals i.e., stores the value of Rx into memory which is formed from adding contents of Ry and an offset.

For each microstate, write the control signals used. Signals irrelevant to the state can be omitted and will be assumed to be zero. **You will lose points for an inefficient answer!** An example answer can be found below. *Note the use of RegSel instead of regno!*

Example: **ADD** instruction

ADD0: DrREG, LdA, RegSel=01

ADD1: DrREG, LdB, RegSel=10, BrSel = 0

ADD2: DrALU, WrReg, func=00, RegSel=00

Enter your microstates of the **SW** instruction for the LC-5000 below:

sw0: RegSel = 01, DrREG, LdA, BRSel = 1, LdB

sw1: func = 00, DrALU, LdMAR

sw2: RegSel = 00, DrREG, WrMEM

Q1.2 BEQ microcode

20 Points

Write out the microstates for an efficient `BEQ` instruction that makes use of the modifications on the LC-5000 datapath. For each microstate, write the control signals used. Signals irrelevant to the state can be omitted and will be assumed to be zero. **You will lose points for an inefficient answer!**

You should write out the full logic for `BEQ`; this means including the microstates for when a branch is taken. You should assume that asserting `ChkCmp` at the correct time will select the correct next state for the branch; and you should assume that the branch **is taken** in order to write out the full logic for `BEQ`.

Enter your microstates of the `BEQ` instruction for the LC-5000 below:

BEQ0: RegSel = 00, DrReg, LdA
BEQ1: RegSel = 01, DrReg, BrSel = 0, LdB
BEQ2: func = 01, DrALU, LdCR, ChkCmp = 1
BEQ4: DrPC, LdA, BRSel = 1, LdB
BEQ5: func = 00, DrALU, LdPC

Q2 Datapath Design

16 Points

In datapath design, some approaches are to use a single bus design or dual-bus design.

Q2.1 LC 2200 Bus Design

4 Points

What type of bus design does the LC-2200 have?

☒ Single-bus

☐ Dual-bus

Q2.2 Single-Bus vs Dual-Bus Design

12 Points


Describe one benefit of having a single-bus design AND one drawback of having a single-bus design.

Benefit: one benefit is that there are less connections between items through wires which is less expensive

Drawback: more instructions are necessary to move around many pieces of data between multiple components since only one can be on the bus per clock cycle

Q3 Microcontroller Design

22 Points

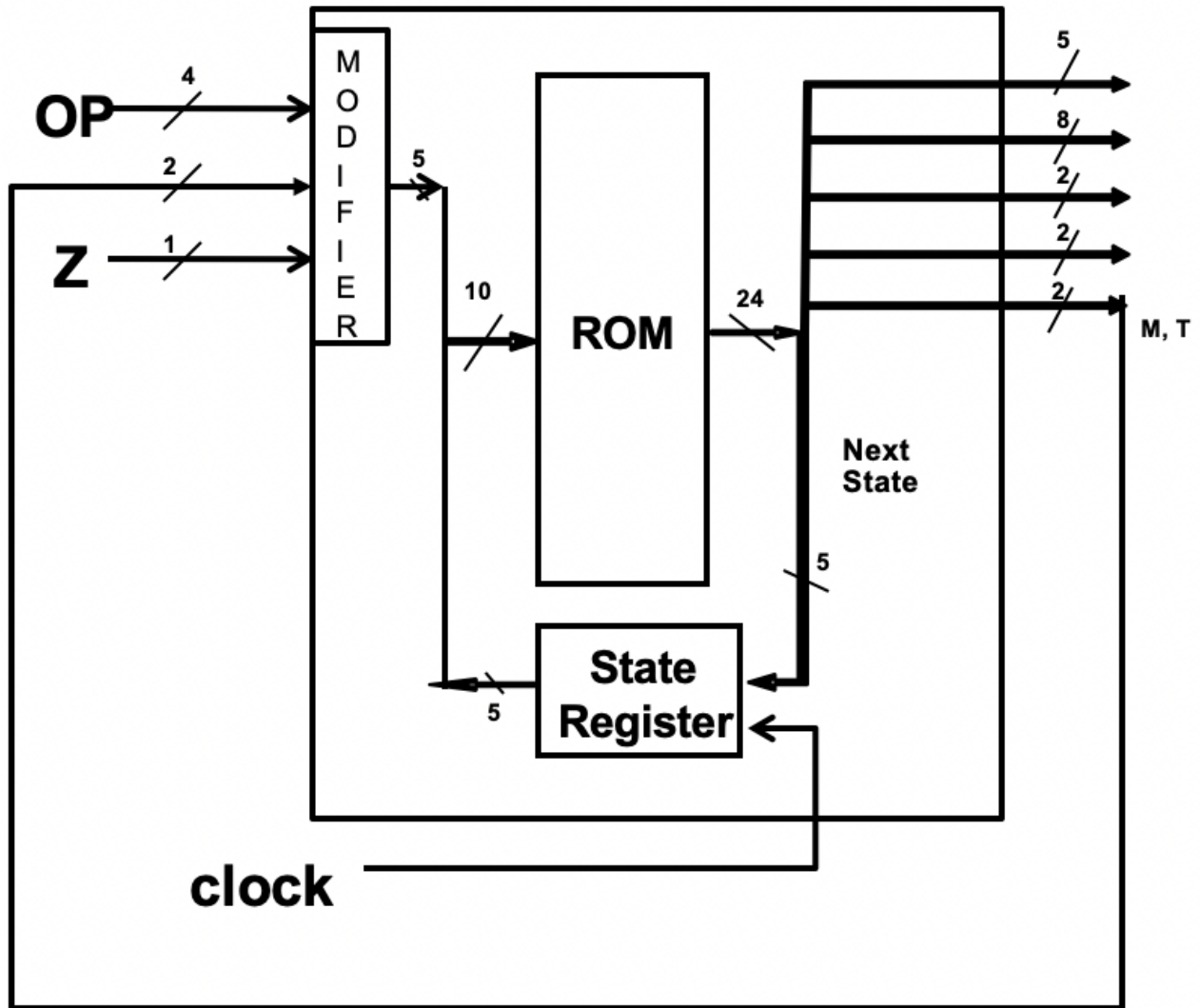

Consider the Flat ROM from the LC-2200 microcontroller. The Z-bit is equivalent to CmpOut in the LC-520 (i.e. it tells the microcontroller whether or not to branch).

The bit layout of the input to the rom looks like this:

MSB | --- 4 bit OP --- | --- 1 bit Z --- | --- 5 bit State --- | LSB

Q3.1 Fetch microstates

4 Points

Suppose fetch contains 3 microstates (fetch1 starts at *00001*), and the base address for next state is *00000*. What is the address in ROM that stores the fetch3 and lw1 respectively?

fetch3

0000000011

lw1

0011000000

Q3.2 BEQ microstates

6 Points

Assume BEQ has 6 microstates in total (3 microstates to compare register values and 3 microstates to jump to new address), denote them as *beq1*, *beq2*, ..., *beq6*. At which microstate(s) will we turn on the T bit?

Beq 4

Q3.3 M bit

8 Points

Describe the reason why we have a M bit

We have an m-bit to tell whether we should "enable" the opcode to determine the opcode to determine the next address. When $M=1$, we will move to the execution of the next instruction whereas when $M=0$, we will be in the Fetch and Decode phases and won't move onto the next instruction written. If M is enabled, then the Mbit and opcode become 7-10 address bits.

Q3.4 Minimum bitsize of Next State Register

4 Points

Assume the following:

- Fetch takes 3 microstates
- Any individual instruction, except for BEQ, takes at most 4 microstates
- The first half of branch takes 3 microstates
- The second half of branch takes 3 microstates (for a total of 6 branch microstates)

What is the smallest acceptable size of the Next State register in bits?

- ☐ 1
- ☐ 2
- ☐ 3
- ☐ 4
- ☒ 5

Q4

6 Points

For each of the six examples below:

- choose whether it is synchronous or asynchronous
- choose whether it is an exception, trap, or interrupt

Q4.1

1 Point

Keyboard inputs is a(n) ____ event.

- ☐ Synchronous
- ☒ Asynchronous

This would be an example of a(n) ____.

- ☐ Exception
- ☐ Trap
- ☒ Interrupt

Q4.2

1 Point

Indexing an array outside of its bounds is a(n) ____ event.

- ☒ Synchronous
- ☐ Asynchronous

This would be an example of a(n) ____.

- ☒ Exception
- ☐ Trap
- ☐ Interrupt

Q4.3

1 Point

Making a System Call is a(n) ____ event.

- ☒ Synchronous
- ☐ Asynchronous

This would be an example of a(n) ____.

- ☐ Exception
- ☒ Trap
- ☐ Interrupt

Q4.4

1 Point

Receiving a printer finished message is a(n) ____ event.

- ☐ Synchronous
- ☒ Asynchronous

This would be an example of a(n) ____.

- ☐ Exception
- ☐ Trap
- ☒ Interrupt

Q4.5**1 Point**

Floating point underflow is a(n) ____ event.

- ☒ Synchronous
- ☐ Asynchronous

This would be an example of a(n) ____.

- ☒ Exception
- ☐ Trap
- ☐ Interrupt

Q4.6**1 Point**

Writing to a file is a(n) ____ event.


- ☒ Synchronous
- ☐ Asynchronous

This would be an example of a(n) ____.

- ☐ Exception
- ☒ Trap
- ☐ Interrupt

Q5 System vs. User Stack

3 Points

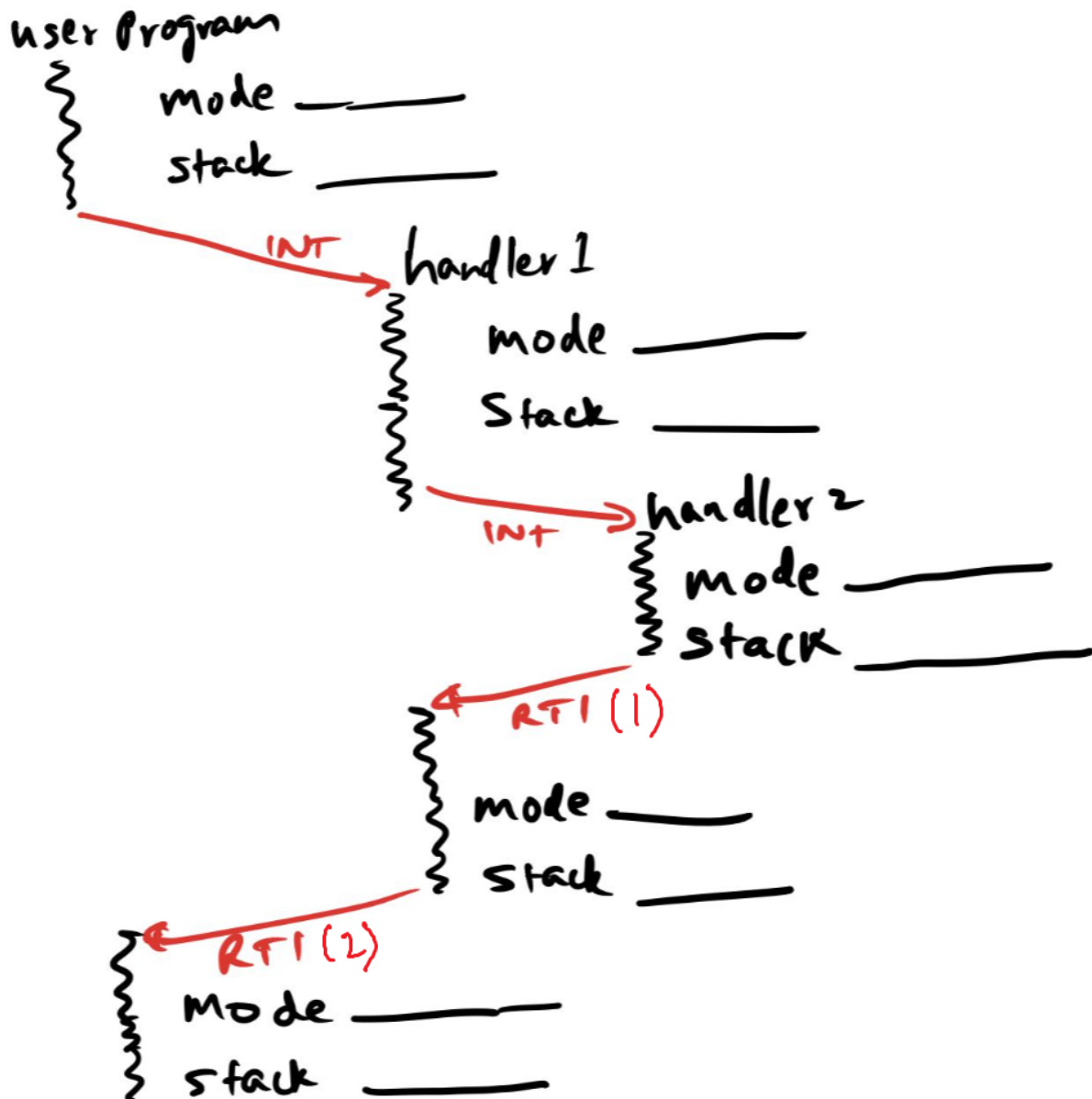

Fill in the blanks (in questions 5.1 to 5.3) to indicate the mode (**user, kernel**) of the processor and the state (**user, system**) of the stack. The squiggly black lines indicate a program, and the red arrows indicate a change in what program is executing (with a label indicating what operation is happening).

Q5.1 User Program

1 Point

What mode is the processor in?

- ☒ User
- ☐ Kernel

What state is the stack in?

- ☒ User
- ☐ System

Q5.2 Handler 1

1 Point

What mode is the processor in?

- ☐ User
- ☒ Kernel

What state is the stack in?

- ☐ User
- ☒ System

Q5.3 After RTI(2)

1 Point

What mode is the processor in?

- ☒ User
- ☐ Kernel

What state is the stack in?

- ☒ User
- ☐ System